
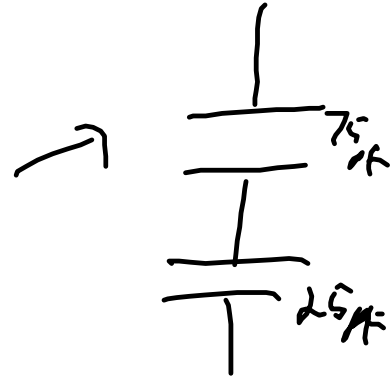


P472 Q28 Cambridge study guide

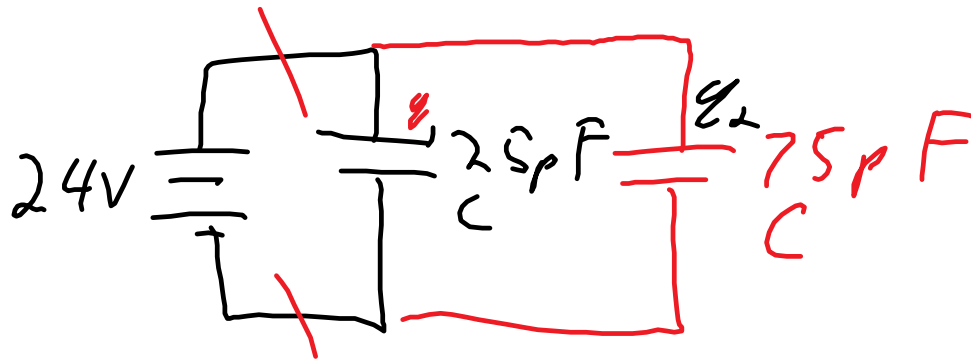

$$C = \frac{Q}{V} \quad Q = CV = 25 \text{ pF} \times 24 \text{ V} = 600 \text{ pC}$$

$$V = \frac{Q}{C}$$

$$V_1 = V_2$$

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

$$Q_1 + Q_2 = Q_0$$

$$\begin{aligned} \text{Energy} &= \frac{1}{2} C_1 V^2 + \frac{1}{2} C_2 V^2 \\ &= \frac{1}{2} C_1 V_0^2 \end{aligned}$$

$$\frac{1}{2} 25 \text{ pF} \times (24 \text{ V})^2 = 7200 \text{ pJ}$$

7.2 nJ

$$\frac{(q_1 - q_2)}{C_1} = \frac{q_2}{C_2}$$

$$\frac{600 \text{ pC} - q_2}{25 \text{ pF}} = \frac{q_2}{75 \text{ pF}}$$

$$600 \text{ pC} - q_2 = \frac{1}{3} q_2$$

$$q_2 = 450 \left(\frac{3}{4} \right) \text{ pC}$$

$$q_2 = \underline{450 \text{ pC}}$$

$$q_1 = \underline{150 \text{ pC}}$$


$$E_{\text{avg}} = \frac{1}{2} (25 \text{ pF}) \left(\frac{150 \text{ pC}}{25 \text{ pF}} \right)^2 + \frac{1}{2} (75 \text{ pF}) \left(\frac{450}{75} \right)^2$$


$$= 450 \mu\text{J} + 1350 \mu\text{J}$$

$$= 1800 \mu\text{J}$$

$$\begin{array}{r} 7200 \mu\text{J} \\ - 1800 \mu\text{J} \\ \hline 5400 \mu\text{J} \end{array} \quad \checkmark$$

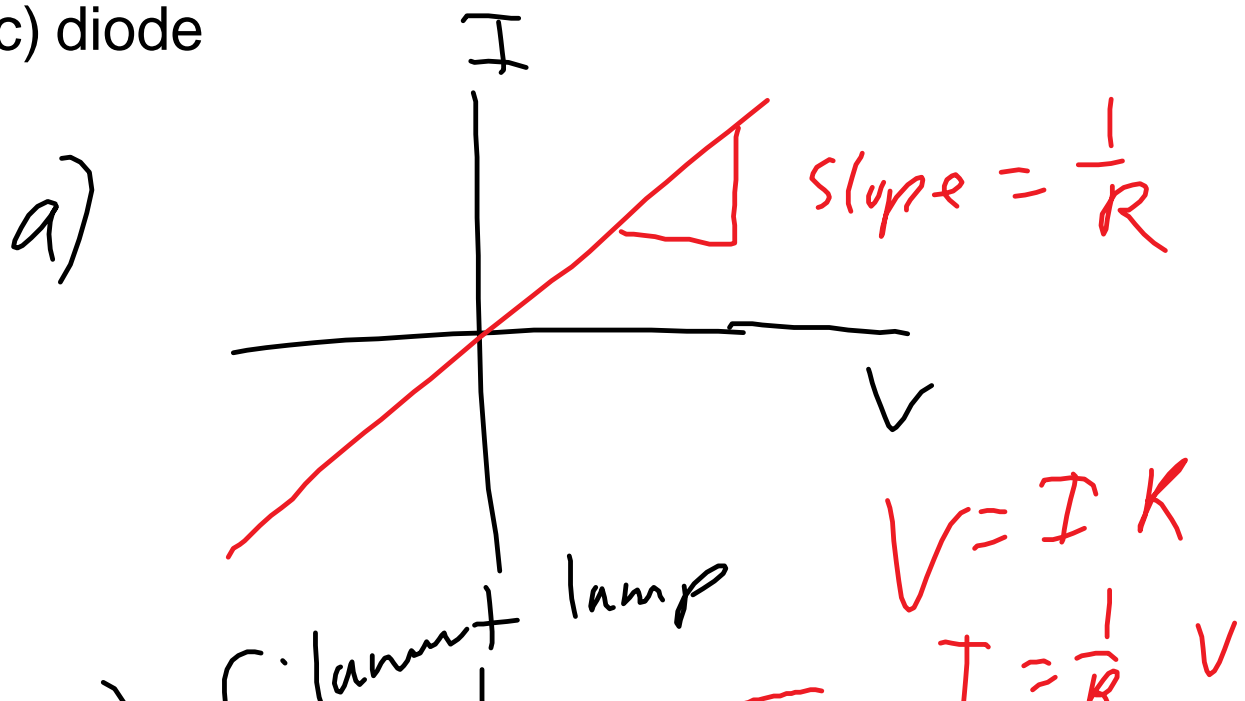- Draw the I vs V graph for
- a) An ohmic device (resistor)
 - b) A filament light bulb
 - c) diode



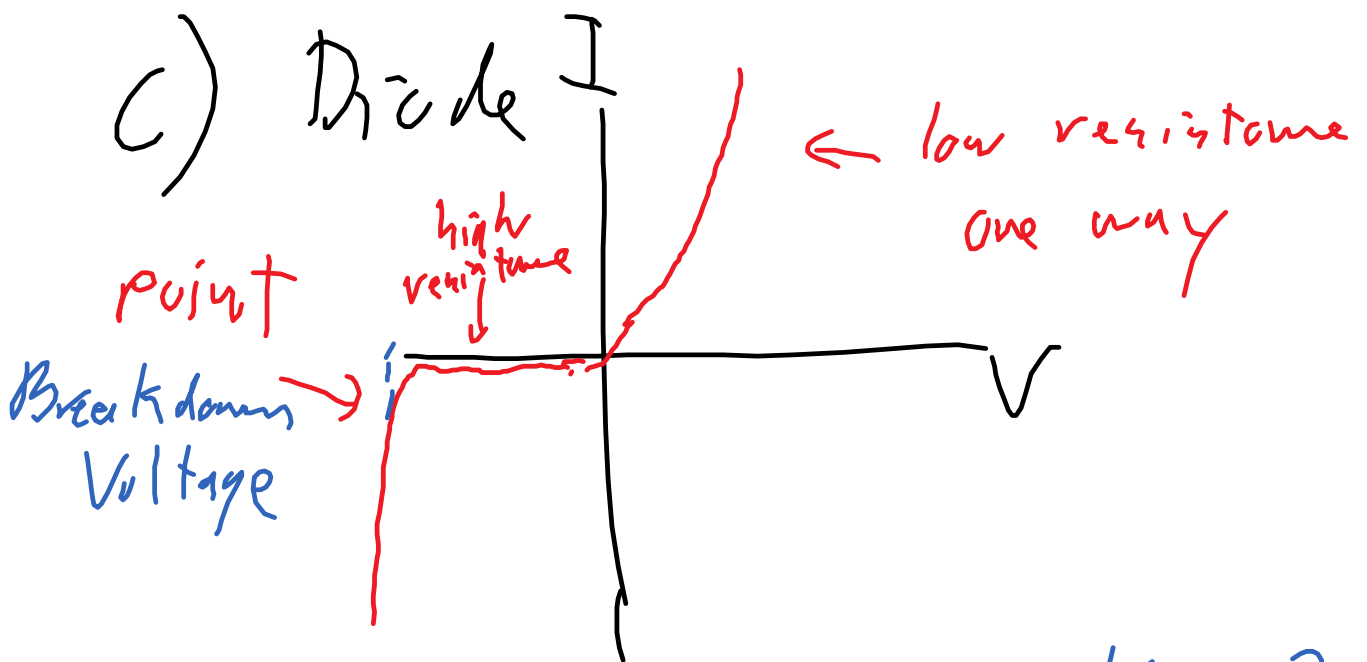

Why do diodes do this?
 How can we use this?

AC \rightarrow DC
 Converter
rectification


doping

You build a diode using a semiconductor with different compounds embedded - this process of embedding materials is called doping.


If you embed a material that lacks an electron in the outer orbit, it is called a "hole" because electrons will tend to go into the hole.

If you embed a material with extra electron in the outer orbit, it will tend to give off electrons.

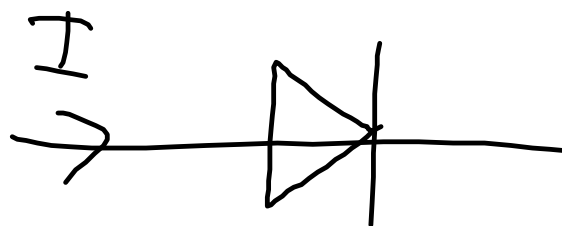Boundary between the two different materials, creates a potential boundary - prevents current from going towards the extra electrons.





low resistance

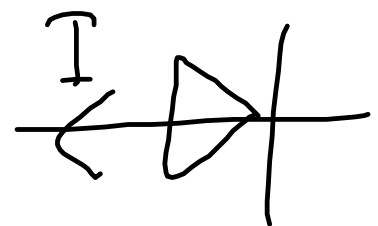


high resistance




AC supply

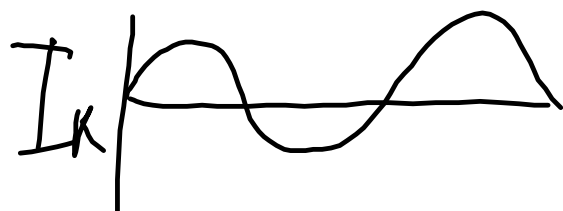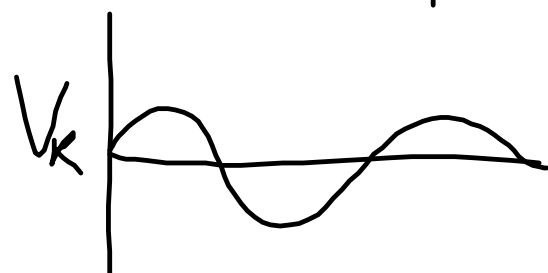


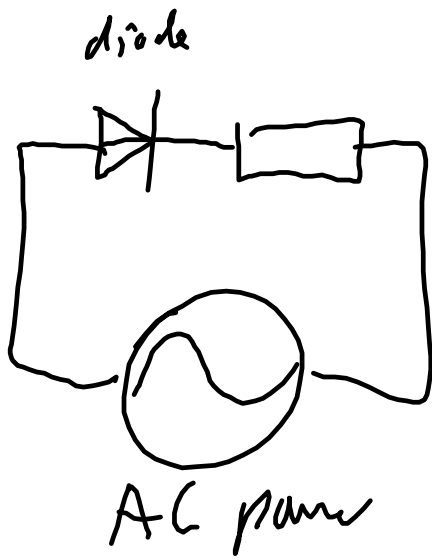


$\frac{1}{R}$

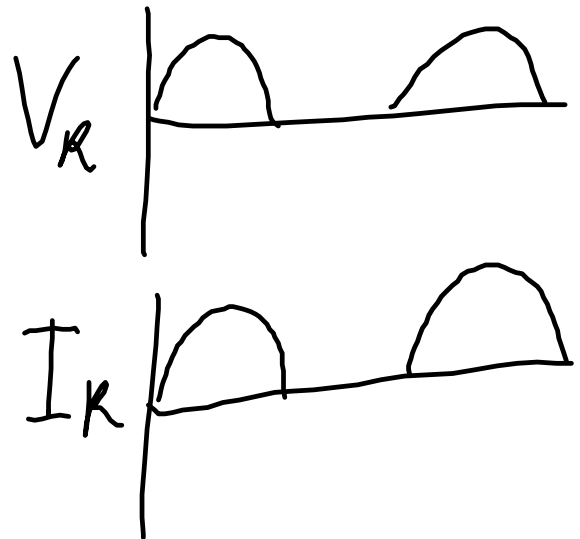

p455 → handout

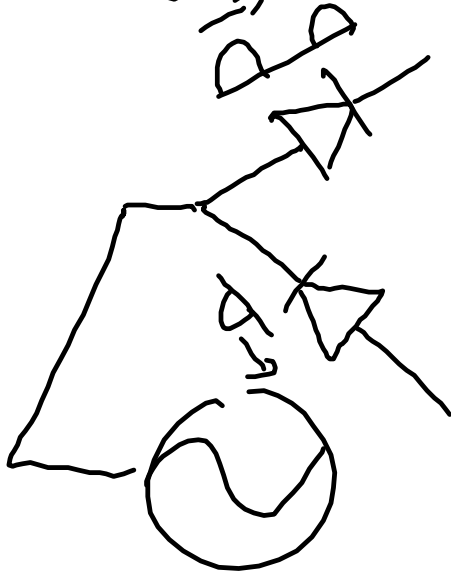

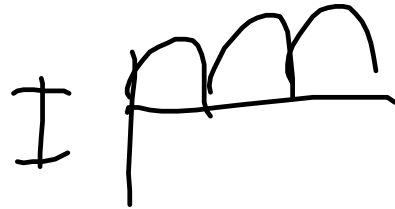


add a
capacitor
to delay the
current and
smooth out
the signal


P470

P472 Q35


<https://www.youtube.com/watch?v=cyhzpFqXwdA>

Video on rectifiers

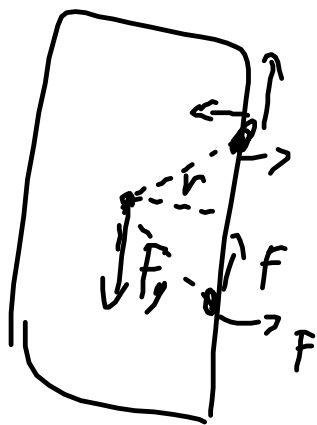

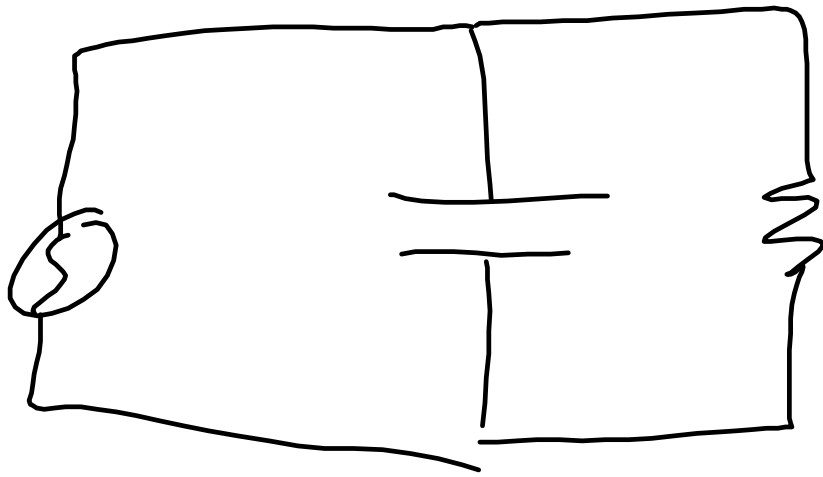

Q28 p 472 Cambridge

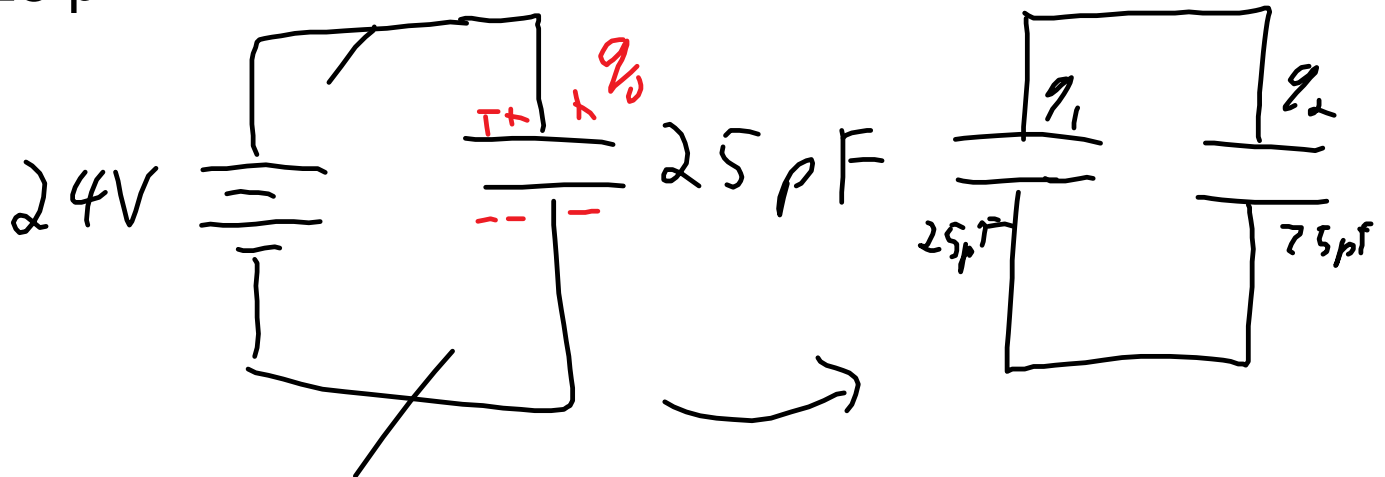

$$C = \frac{q}{V} \quad q_0 = CV = 24V \times 25 \text{ pF} = 600 \text{ pC}$$

$$\begin{array}{ccc} V_1 & = & V_2 \\ q_1 & & q_2 \end{array} \quad \begin{array}{ccc} q_1 + q_2 & = & q_0 \\ (q - q) & & q \end{array}$$

$$\frac{q_1}{C_1} = \frac{q_2}{C_2}$$

C_1

C_2

$$\frac{(600 \text{ pC} - q_2)}{25 \text{ pF}} = \frac{q_2}{75 \text{ pF}}$$

$$600 \text{ pC} = 4 q_2$$

$$q_2 = 150 \text{ pC} \quad q_1 = 150 \text{ pC}$$

$$b) \text{ Energy} = \frac{1}{2} C V^2 = \frac{1}{2} 25 \text{ pF} (24 \text{ V})^2 = 7200 \text{ pJ}$$

$$\text{Energy final} = \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2$$

$$\frac{1}{2} 25 \text{ pF} \left(\frac{150 \text{ pC}}{25 \text{ pF}} \right)^2 + \frac{1}{2} (75 \text{ pF}) \left(\frac{450 \text{ pC}}{75 \text{ pF}} \right)^2$$

$$450 \text{ pJ} + 1350 \text{ pJ}$$

$$= 1800 \text{ pJ}$$

$$I_{\text{loss}} = 7200 \text{ pJ} - 1800 \text{ pJ}$$


$$= \boxed{5400 \text{ pJ}}$$


Diodes:

Doped and Rekt

Draw the I vs V graph for

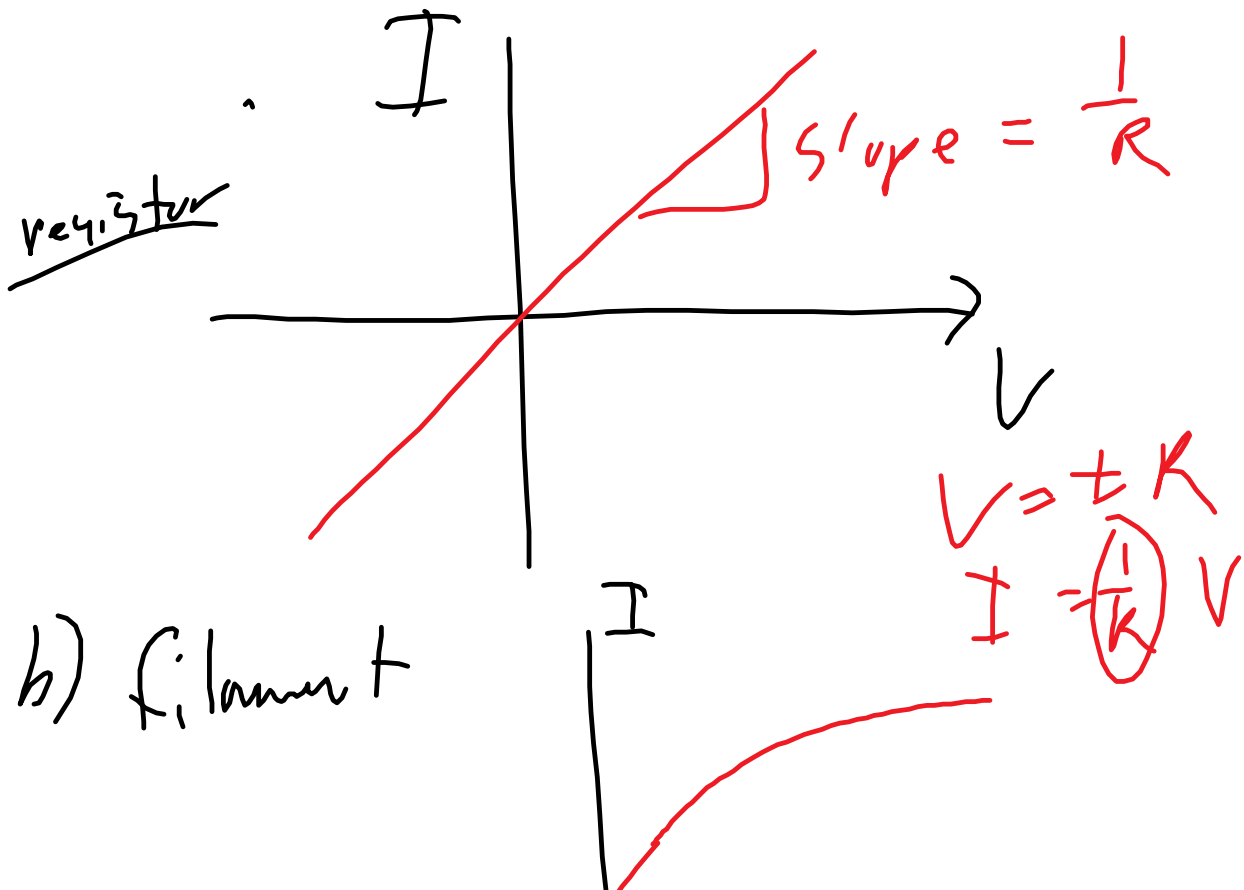- a) An ohmic device (resistor)
- b) A filament light bulb
- c) A diode



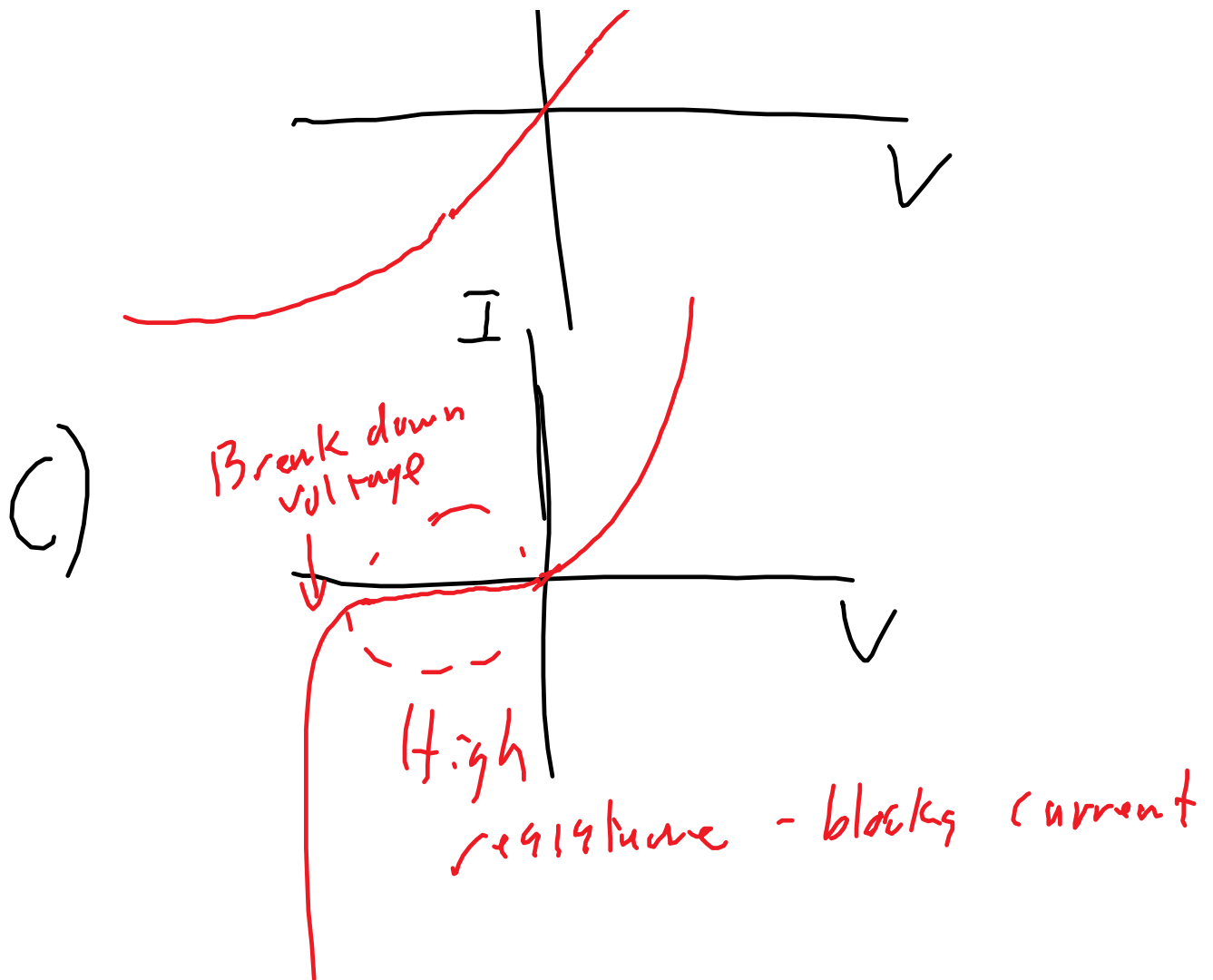

Why do diodes do that?
How can we use that?








Diodes are made from semi-conductors with 2 parts with compounds embedded in the material - called doping.


Silicon is a semi-conductor and if you add a material that has room for electrons in the outer orbital, it can create a "hole" that attracts electrons. p-type

If a material has a free electron in the outer

orbital, it can give off electrons easily. n-type

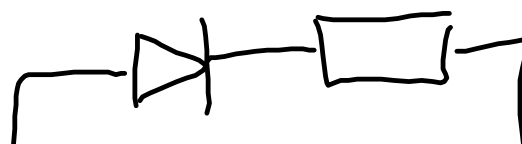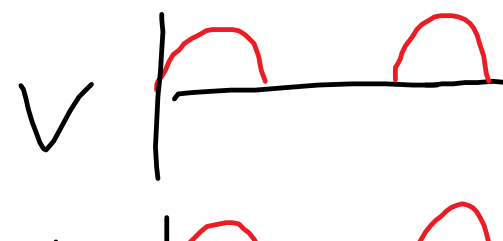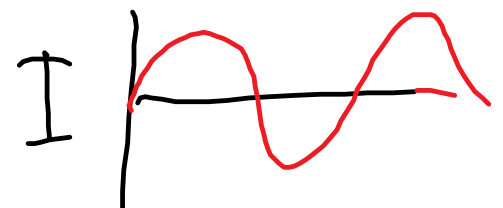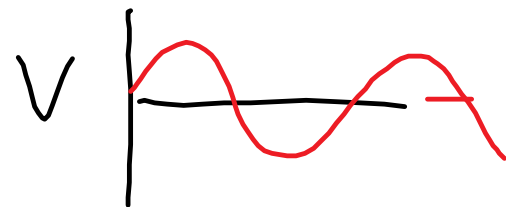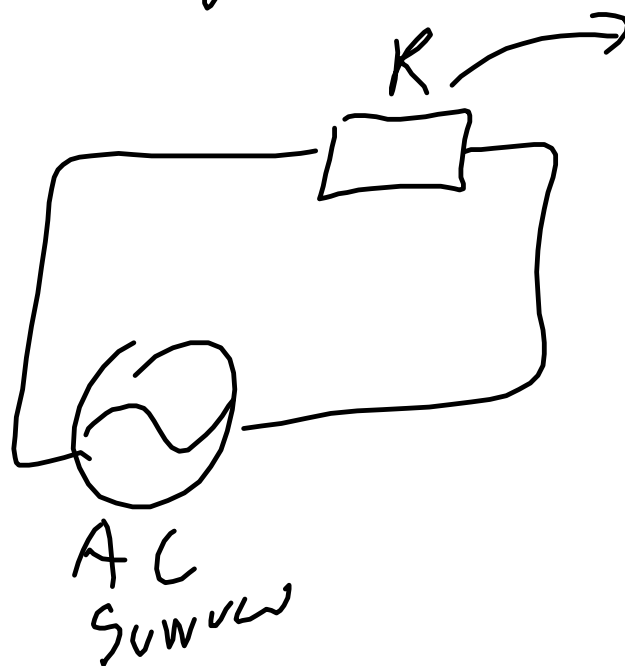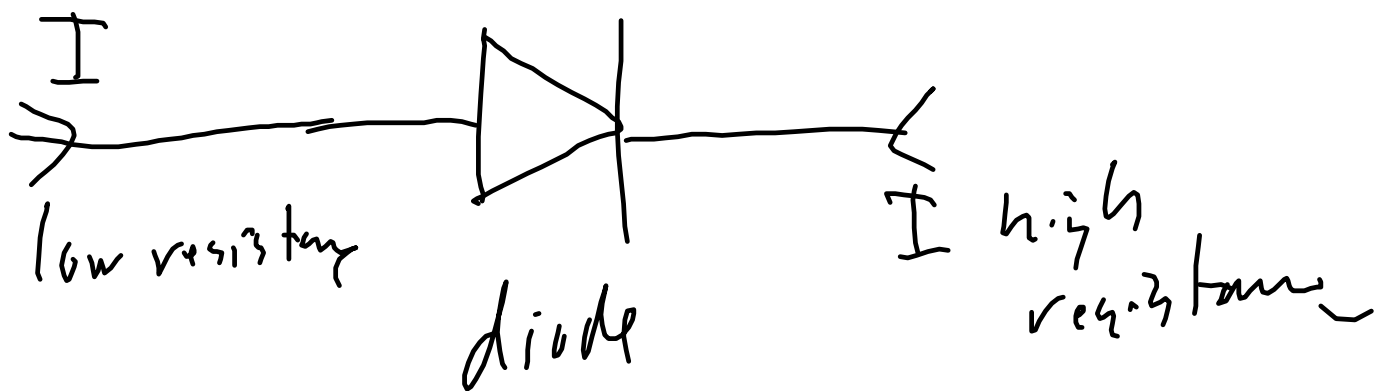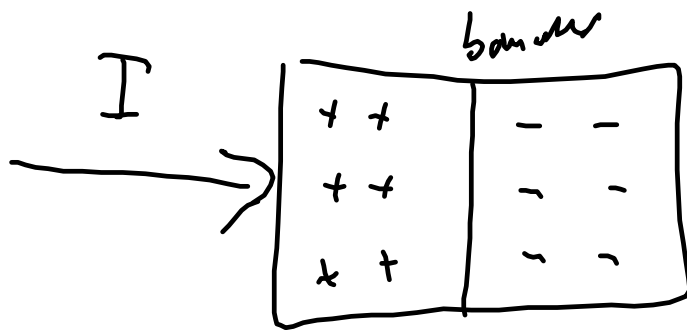At the medium boundary between the two doped substances, there is a potential boundary that allows current to flow one way but not the other.



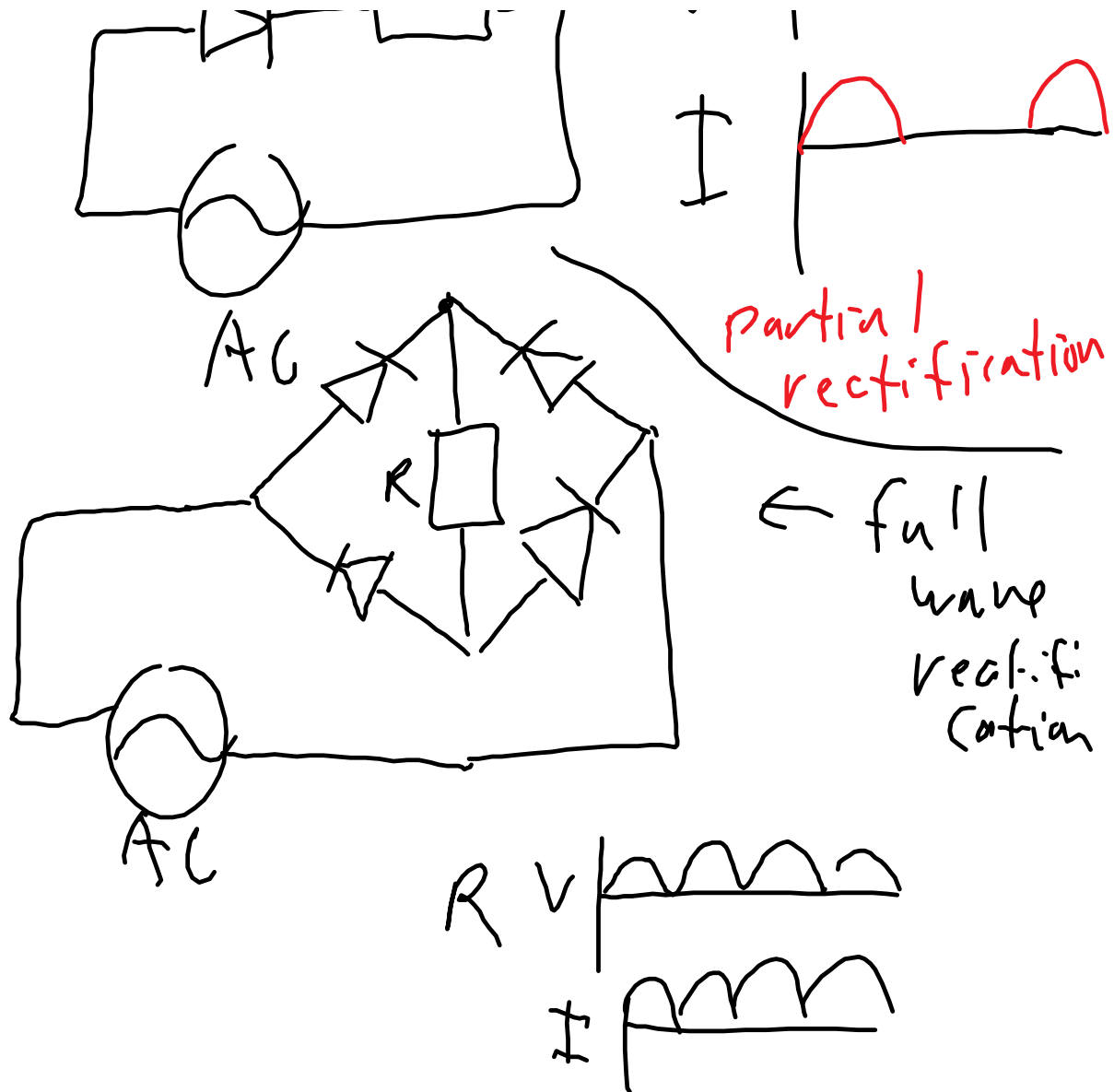

add a capacitor to smooth out the

Signal

P470

